

IEP Design Project – Sound to Light


Lakee Sivaraya

CRSid : ls914

Lab Group : 53

6 March 2021

Emmanuel College

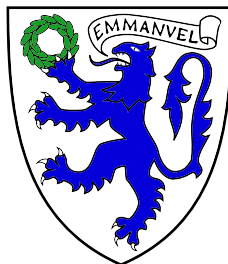

1 Introduction

The goal of the IEP Design Project was to design a **VU meter** to visualize the amplitude of audio signals measured with a microphone. This lab report discusses the approach taken to design and build the device on a breadboard.

2 Design

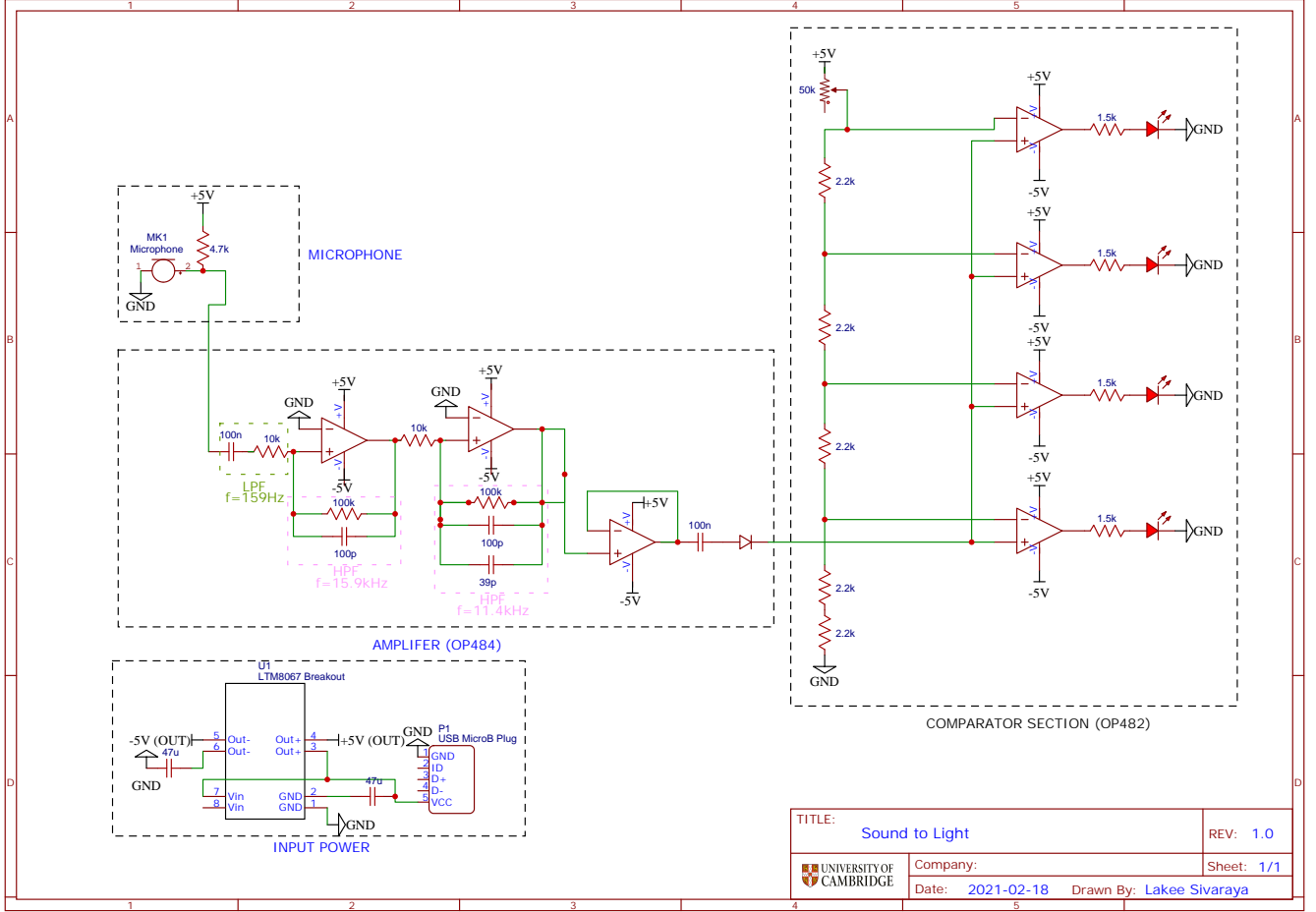


Figure 1: Schematic of design split up into functional components

2.1 Input Power

The LTM8067 break out board was used to provide the +5V and -5V rails required to properly bias the OpAmps used in this circuit since they do not operate without a bipolar supply. 47μF capacitors were placed between the rails to reduce noise.

2.2 Microphone

The microphone has an internal FET, so a 4.7kΩ pull up resistor was connected between the “drain” and +5V rail to power the microphone and provide some amplification.

2.3 Amplifier

With a 1kHz sine test tone, it was found that the output of the microphone had an amplitude of ~ 5mV. To get this voltage higher, the OP484 was used to chain two non-inverting amplifiers with individual gains of $\frac{100k\Omega}{10k\Omega} = 10$ to amplify the microphone signal by a factor $10^2 = 100$.

Using a speaker to play a 1kHz test audio, the output from the amplifier, Figure 2, showed that we got an amplification of around $565.7/5 \approx 113$, which represent a small 13% error from the theoretical gain.

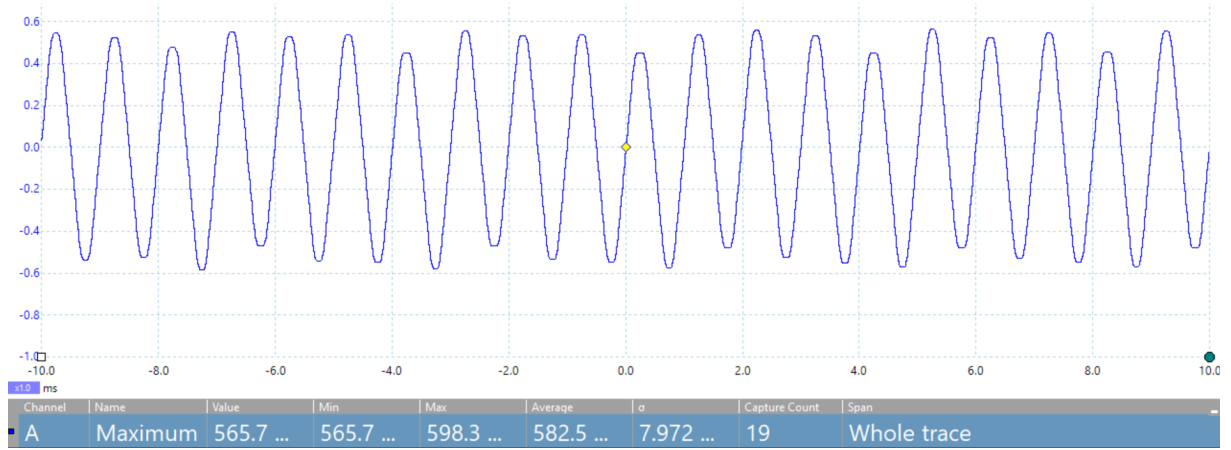


Figure 2: Output signal from a $1kHz$ test sound

High and low pass filters (see Figure 1) were implemented with cutoffs of $f_{c,high} = 159Hz$ and $f_{c,low} = 15.9, 11.4kHz$ respectively. These filters helped massively to filter out the noise (discussed in greater detail in Section 3 - Noise). OpAmp buffer was connected after the OpAmp amplifiers to isolate the amplification section from the comparator section, thus preventing any unnecessary interference. After this buffer a $100nF$ capacitor were used to decouple the signal thus removing the small $0.1V$ DC offset present in the signal. Then the signal was rectified using a diode as we only need to consider the positive voltages in the comparator section.

2.4 Comparator

The comparator section used the 4 OpAmps on the OP482, to compare the input signal from the amplification (which was connected to the $V+$ pin), to a reference voltage (connected to the $V-$ pin). The output of each OpAmp is connected in series with an LED and a $1.5k\Omega$ current limiting resistor. When the signal goes above the reference, the output of the OpAmp goes to $+5V$ thus switches the LED on.

A potential divider was used to create the voltage references. The divider uses a single $50k\Omega$ potentiometer in series with $2.2k\Omega$ resistors to create voltage references of $1.08, 0.86, 0.65, 0.43V$ with the potentiometer was set at $\sim 40k\Omega$. The reason why these voltage references were so high (much greater than $500mV$, see Figure 2):

1. The voltage from real music (not the single frequency test tune) reached peaks of $1V$
2. Noise (Figure 6) has an amplitude of around $0.2V$, meaning my lowest voltage reference should be higher than this

2.5 Breadboard Layout

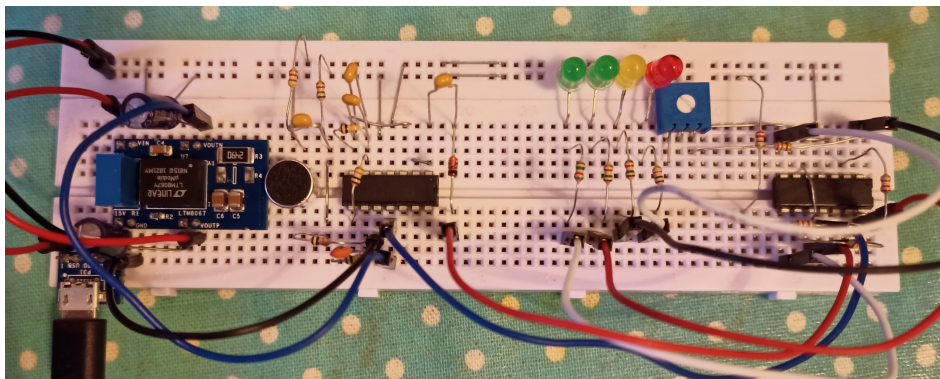


Figure 3: Breadboard Layout

One of the biggest challenge of this project was that we were only allowed to use components from the ADALP2000 kitset, meaning we were restricted to a small breadboard and the excessively long wires in the kitset.

To circumvent this restriction, the metal ends of resistor were used to create connections between the holes, thus reducing the amount of jumper wires need and reduces clutter.

3 Noise

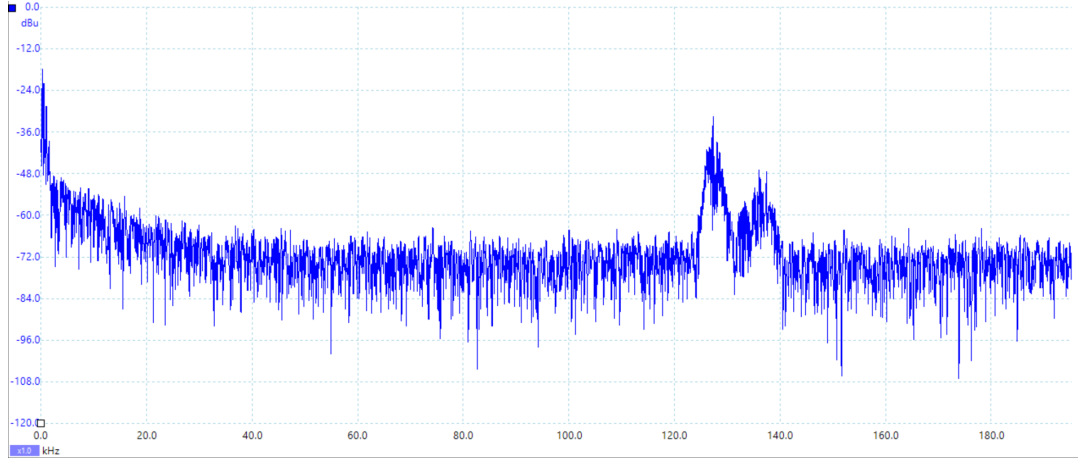


Figure 4: Spectrum analysis of noise

Noise was easily the biggest issue that I faced during this project. From the spectrum in Figure 4 we can see that there is a significant high frequency noise at around 130kHz . The source of this noise is the transformer in the LTM8067 break out board. The strategies used to minimize the noise were:

1. $47\mu\text{F}$ capacitors between the rails of the supply “smoothing” out the noise.
2. RC Low pass filters with cutoff frequencies well below the noise frequency to filter out the noise. Figure 5 shows how powerful a simple RC low pass filer can be at removing the high frequencies from the noisy signal (red) and outputs a fairly clean signal (blue). The cut-off frequencies, f_c of the filters were calculated using the equation,

$$f_c = \frac{1}{2\pi RC}$$

The chosen values of f_c were 15.9kHz , 11.4kHz , these values were chosen as they could be achieved using standard parts available in the kitset, and also most music does not have audio with frequencies higher than 10kHz , which explains the fairly low values for the cutoff frequencies.

Additionally 50Hz noise was present in my signals due to the AC wires in the walls of my room. This noise is clearly evident in Figure 2 where you can see that there is some low frequency noise causing the sine waves to be slightly offset. To combat this, the signal from the microphone was filtered using an RC high pass filter with $f_c = 159\text{Hz}$.

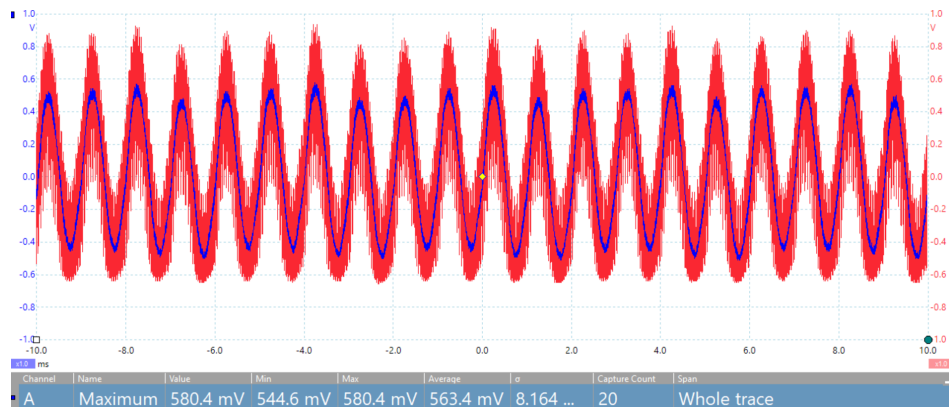


Figure 5: Filtering of the noise

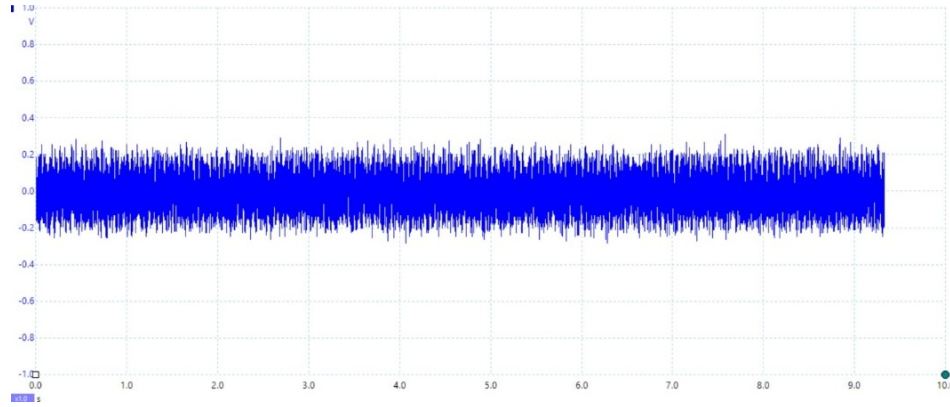


Figure 6: Noise left after filtering (Timebase: $1s/div$)

The strategies used to filter out the noise worked very well, however the noise did not completely disappear, leaving me with a $0.2V$ noise (Figure 6).

The main lesson learnt was that bipolar supplies should not be near the components that use it.

4 Conclusion

In conclusion, the designed VU meter clearly visualizes music ([video link](#)). The performance of my VU meter is the best that could be achieved with all the components that I have access to and the limited space for design. Noise caused many issues initially, but the strategies mentioned in Section 3 - Noise minimized its impact on the performance of my VU meter.